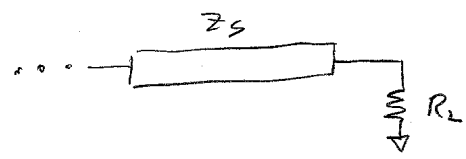






① $\Gamma_L = \frac{Z_L - Z_S}{Z_L + Z_S}$, $Z_S = 50\Omega$

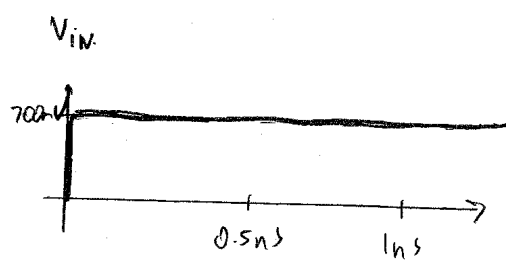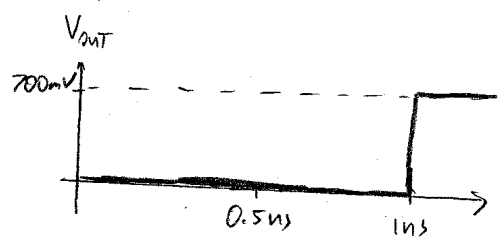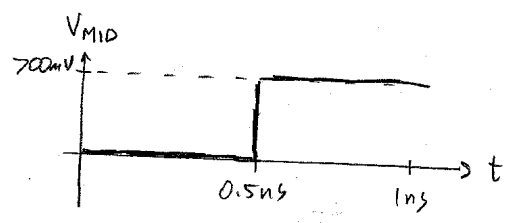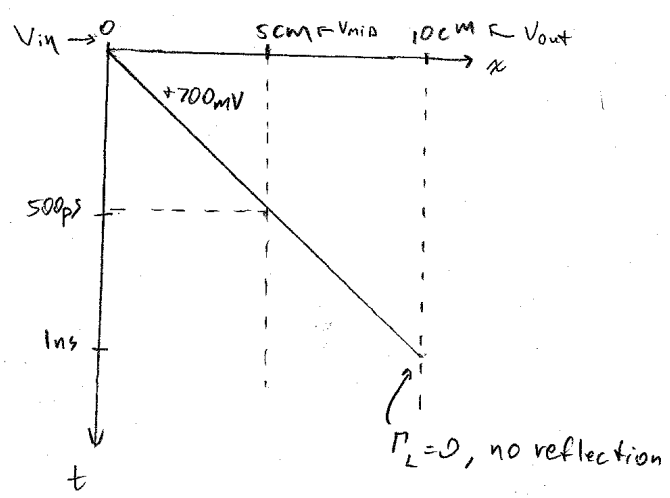- a) $Z_L = 10\Omega$, $\Gamma_L = -0.67$
- b) $Z_L = 50\Omega$, $\Gamma_L = 0$
- c) $Z_L = 200\Omega$, $\Gamma_L = 0.6$








② case CAIB)
 $Z_L = Z_0 \rightarrow \Gamma_L = 0$

$\tau = 10\text{cm} / 10^8\text{m/s} = 1\text{ns}$
 $\tau_{\text{mid}} = 5\text{cm} / 10^8\text{m/s} = 0.5\text{ns}$



CASE CID

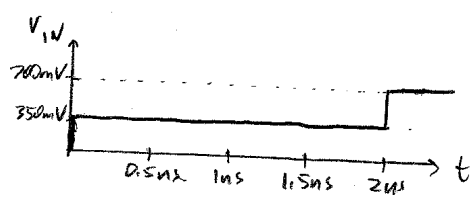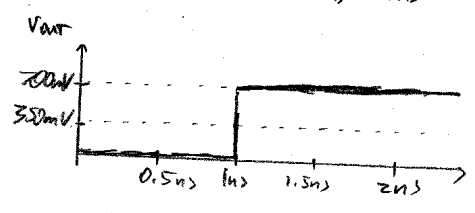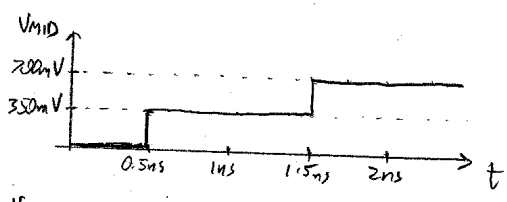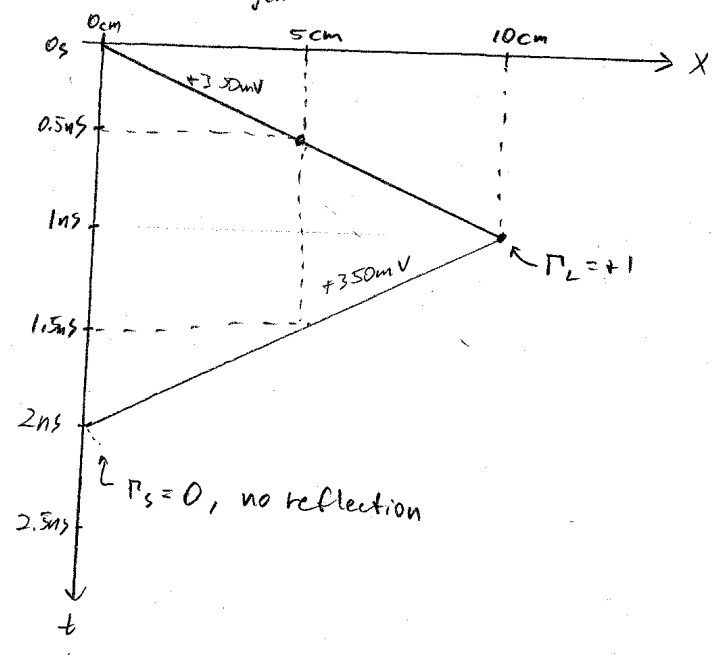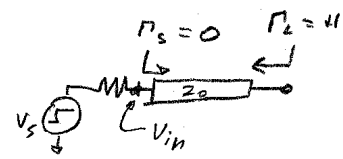$Z_L = \infty \rightarrow \Gamma_L = +1$
 $Z_S = Z_0 \rightarrow \Gamma_S = 0$
 $V_{in} = \frac{Z_0}{Z_0 + R_{gen}} V_S = \frac{1}{2} V_S = 350\text{mV}$



② - continued -

Comments: For driving a digital-bus, it is generally desired to have a single rising edge of the maximum magnitude. This favors load-side termination (Case A/B). With source-side termination V_{in} has two rising edges and takes longer to reach full magnitude.


③ $Z_0 = 100 \Omega$, $\tau = 1 \text{ ps}$, $V_{gen} = 1 \text{ V step}$

Case A

$R_L = R_{gen} = 1 \text{ k}\Omega$


$\Gamma_L = \Gamma_S = 0.818$

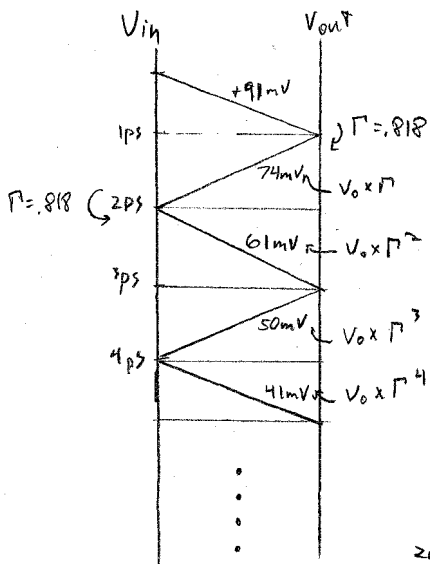$\Gamma_G = -0.818 \rightarrow V_{in}(t=0) = \frac{Z_0}{Z_0 + R_g} V_0$
 $V_{in}(t=0) = 91 \text{ mV} = V_0$




$V_{in} = V_0 (1 + (\Gamma + \Gamma^2) + (\Gamma^3 + \Gamma^4) + (\Gamma^5 + \Gamma^6) + \dots)$

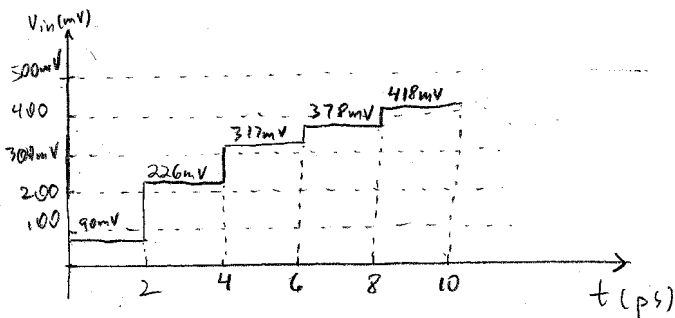$V_{in}(t = \infty) = 500 \text{ mV}$ from Voltage Divider



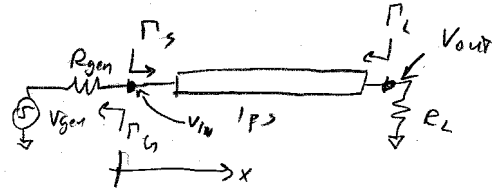
Notice similarity to exponential function



Case B


$R_L = R_{gen} = 10 \Omega$

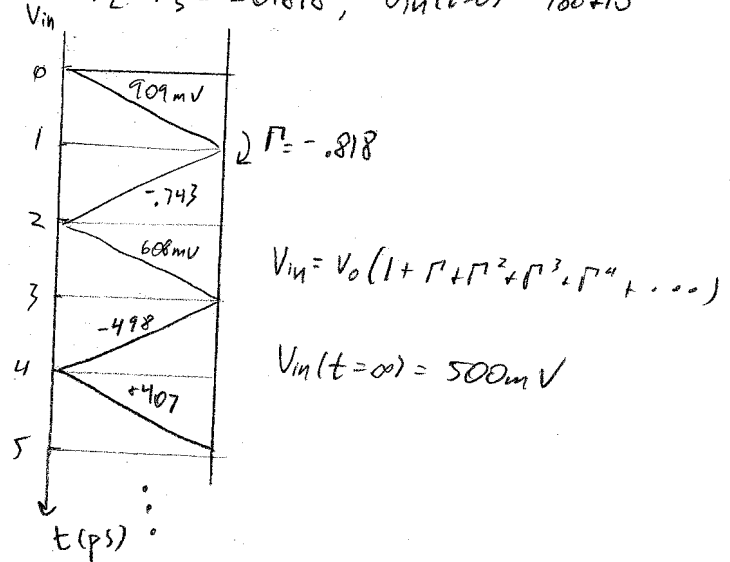$\Gamma_L = \Gamma_S = -0.818$, $V_{in}(t=0) = \frac{100}{100+10} = 909 \text{ mV}$



$V_{in} = V_0 (1 + \Gamma + \Gamma^2 + \Gamma^3 + \Gamma^4 + \dots)$

$V_{in}(t = \infty) = 500 \text{ mV}$

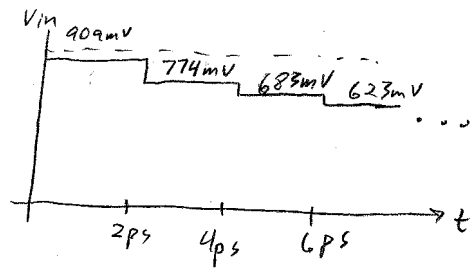

Notice similarity to exponential:






③ - cont. -
 Case C


$R_L = 0 \Omega, R_g = 1k\Omega$

$\Gamma_L = -1, \Gamma_S = +0.818$

$V_o = 91mV$, as before

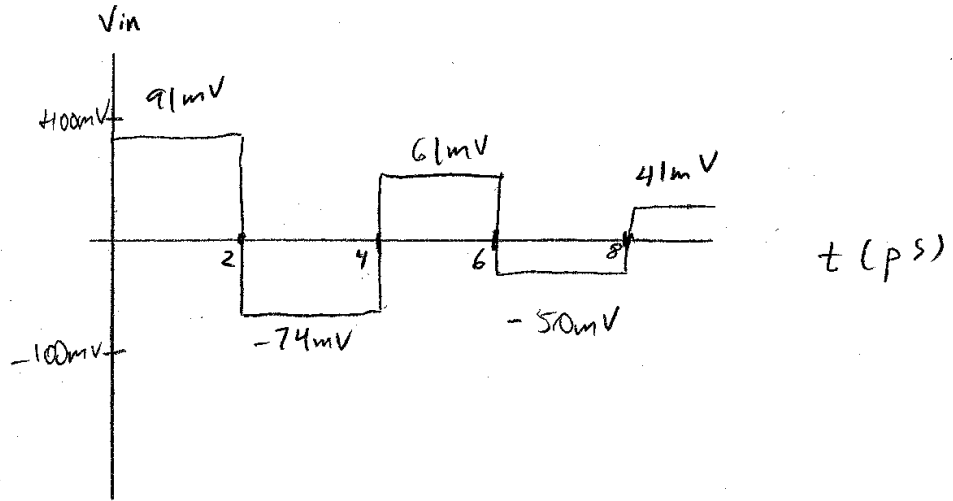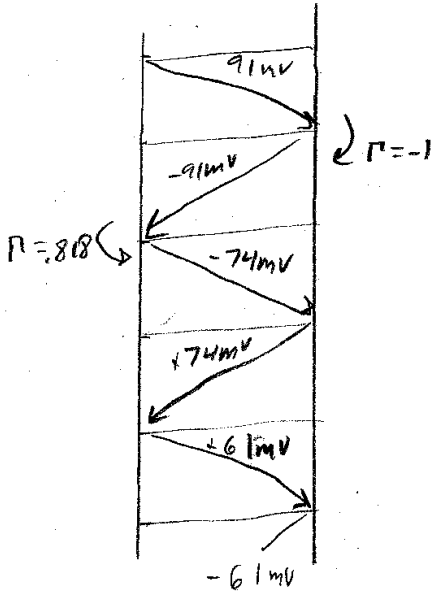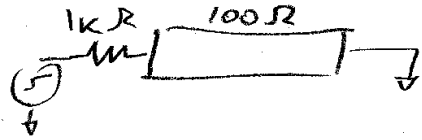

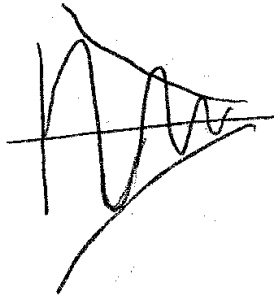Note similarity to exponentially damped oscillation



4

Lumped element model



$$L_T = \alpha Z_0$$

$$C_T = \alpha / c_0$$


$$Z_0 = 100 \Omega, \alpha = 1 \text{ ps}$$

$$\text{So: } L_T = 100 \text{ pH}$$

$$C_T = 10 \text{ fF}$$

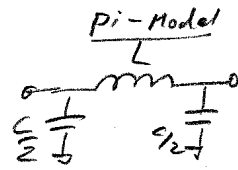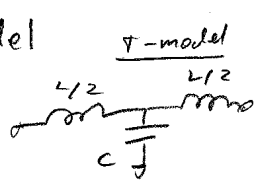

a)

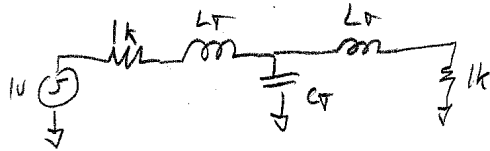


$$R_L = R_g = 1 \text{ k}\Omega$$

$$\tau_{RL} = \frac{50 \text{ pH}}{1 \text{ k}\Omega} = 50 \text{ fs}$$


$$\tau_{RC} = 10 \text{ fF} \times 1 \text{ k}\Omega \parallel 1 \text{ k}\Omega = 5 \text{ ps}$$

$$\tau_{RC} = 100 \times \tau_{RL}$$

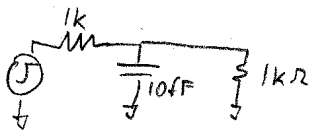
$\tau_{RL} \ll \tau_{RC} \Rightarrow$ Discount inductor effects



Thevenin Equiv.

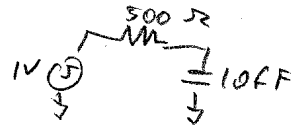

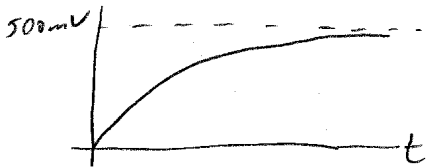
$$V_{in} = (1 - e^{-t/\tau_{RC}}) V_{gen} = \boxed{0.5(1 - e^{-t/5 \times 10^{-12}}) \text{ [V]}}$$



\hookrightarrow Note similarity to prob. 3 a



b) $R_L = R_{gen} = 10 \Omega$

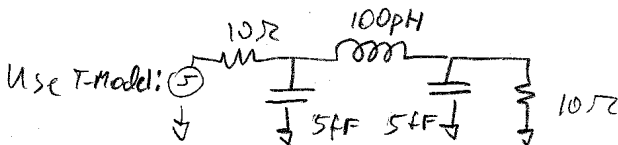

$$\tau_{RL} = \frac{100 \text{ pH}}{20 \Omega} = 5 \text{ ps}$$

$$\tau_{RC} = 5 \text{ fF} \times 10 \Omega = 50 \text{ fs}$$

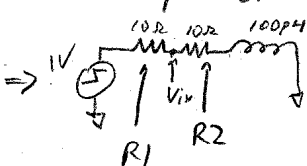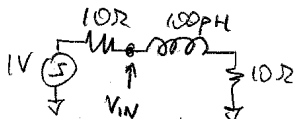$\tau_{RC} \ll \tau_{RL}$ so discount capacitor



$$i(t) = V_{gen}/R (1 - e^{-t/\tau})$$

$$i(t) = 50 \text{ mA} \times (1 - e^{-t/5 \text{ ps}})$$

$$V_{in} = V_{R1} = 1 \text{ V} - 10 \Omega \times i(t)$$




$$\boxed{V_{in} = 1 - 0.5 e^{-t/5 \text{ ps}} \text{ [V]}}$$

\hookrightarrow Note similarity to prob. 3 B

(4) - cont. -

) $R_L = 0 \Omega$, $R_{gen} = 1k\Omega$

Use Pi-Model:

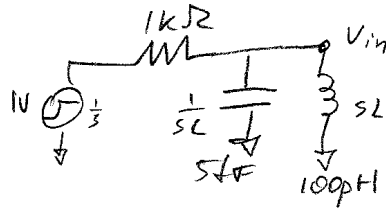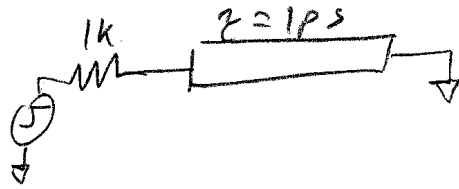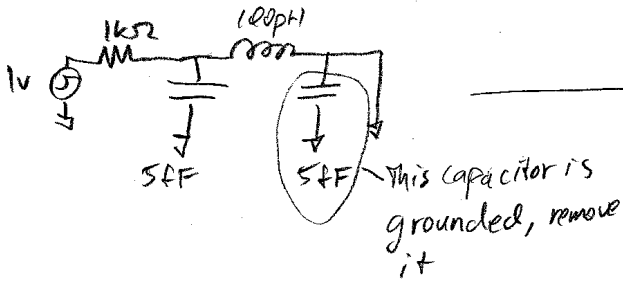

We have a resonator

Nodal analysis in Laplace domain


$$V_{in} sC + \frac{V_{in}}{sL} + \frac{V_{in} - V_{gen}/s}{R} = 0$$

$$V_{in} s^2 LC + V_{in} + \frac{V_{in} sL}{R} = \frac{V_{gen} L}{R}$$

$$V_{in} = \frac{V_{gen} L / R}{s^2 LC + s \frac{L}{R} + 1} = \frac{A}{\omega_n^2 + \frac{2\zeta}{\omega_n} s + 1}$$


$$\omega_n = \frac{1}{\sqrt{LC}}, \quad \zeta = \frac{1}{2R} \sqrt{\frac{L}{C}} = .07$$

↳ Very underdamped

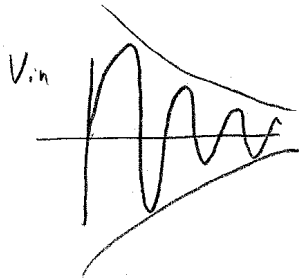

Note similarity to problem 3C

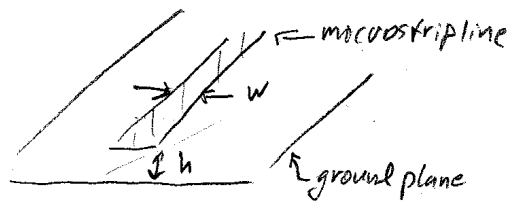⑤ $l = 300 \mu\text{m}$, $v_p = c$, $Z_0 = 100 \Omega$
 since $v_p = \frac{c}{\sqrt{\epsilon_r}}$, $\epsilon_r = 1$, $Z = \frac{l}{v_p} = 1 \text{ ps}$



Pozar Eqn 4.206 pp.185: (this can be found from Eqn 2.5.4 in Gonzalez)

$$\frac{W}{h} \approx \frac{8e^A}{e^{2A} - 2} \quad \text{for } \frac{W}{h} < 2 \quad \text{and } A = \frac{Z_0}{60} \sqrt{\frac{\epsilon_r + 1}{2}} + \frac{\epsilon_r - 1}{\epsilon_r + 1} \left(0.23 + \frac{0.11}{\epsilon_r} \right)$$

$$= 5/3$$

$\frac{W}{h} = 1.63$

(if $\frac{W}{h} < 2$ is a good assumption)

so if we assume $h = 30 \mu\text{m}$ then $W = 49 \mu\text{m}$

$$L_T = Z Z_0 = 1 \text{ ps} \times 100 \Omega = 0.1 \text{ nH}$$

$f_{\text{max}} = \frac{1}{Z} = 1 \text{ THz}$, the freq at which $\lambda = l$. see plot.

⑥ $C_T = Z / Z_0 = 10 \text{ fF}$. See Plot.

Conclusion: Transmission lines can be used to approximate ideal inductors and capacitors, but is less accurate at high frequencies. One application is to use a long skinny strip line which acts like an inductor to provide DC-bias instead of using an RF choke. You will use this in Lab 3.