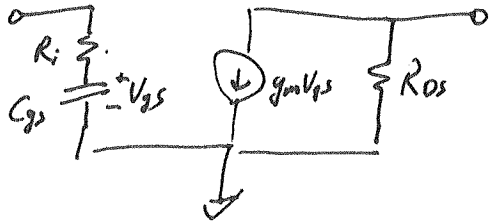


① See HW 5 # 1 for same problem

Find MAG & H21 for unilateral device model
Then calculate f_T , f_{max}



$$g_m = 1 \frac{\text{ms}}{\mu\text{m}} W_g$$

$$R_i = \frac{1}{g_m} = \frac{1000 \Omega}{\mu\text{m} \cdot W_g}$$

$$C_{gd} = 0$$

$$C_{gs} = 0.5 \text{ fF}/\mu\text{m} \cdot W_g$$

$$G_{os} = 0.1 \frac{\text{ms}}{\mu\text{m}} W_g \rightarrow R_{os} = 10 \frac{\text{k}\Omega}{\mu\text{m} \cdot W_g}$$

As we have already found, $MAG = \frac{g_m^2 R_{os}}{4\omega^2 C_{gs}^2 R_i}$

All W_g 's
cancel! ↙

$$= \frac{(1 \frac{\text{ms}}{\mu\text{m}} W_g) (\frac{10 \mu\text{m}}{\text{ms}} W_g)}{4\omega^2 (0.5 \frac{\text{fF}}{\mu\text{m}} W_g)^2 (\frac{1 \mu\text{m}}{\text{ms}} W_g)}$$

$$= \frac{1}{(2\pi)^2 f^2 10^{-26}}$$

at f_{max} $MAG = 1$


$$f_{max} = \sqrt{\frac{1}{(2\pi)^2 10^{-26}}} = \boxed{503 \text{ GHz} = f_{max}}$$

$$H_{21} = \frac{g_m}{j\omega C_{gs}} = 1 \omega f_T$$


$$f_T = \frac{g_m}{2\pi C_{gs}} = \frac{1 \text{ ms}/\mu\text{m} \cdot W_g}{2\pi \cdot 0.5 \frac{\text{fF}}{\mu\text{m}} W_g} = \frac{0.001}{\pi \times 10^{-15}} = \boxed{318 \text{ GHz} = f_T}$$

Problem #1

Unilateral Model:

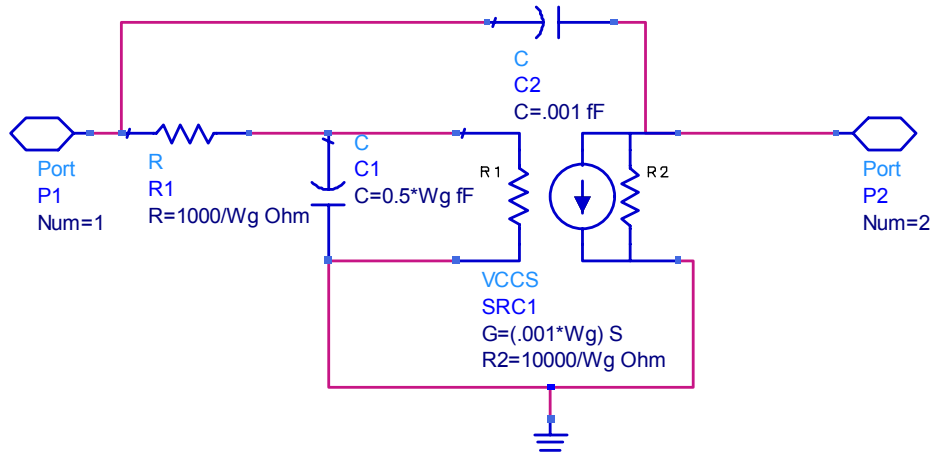


Schematic:

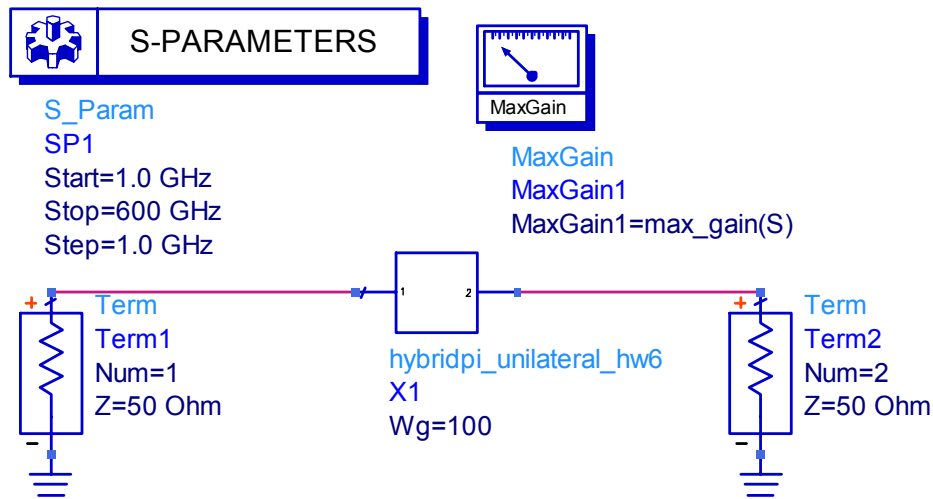

Results:

m2
freq=318.0GHz
dB(H(2,1))=0.008

m1
freq=503.0GHz
MaxGain1=0.005

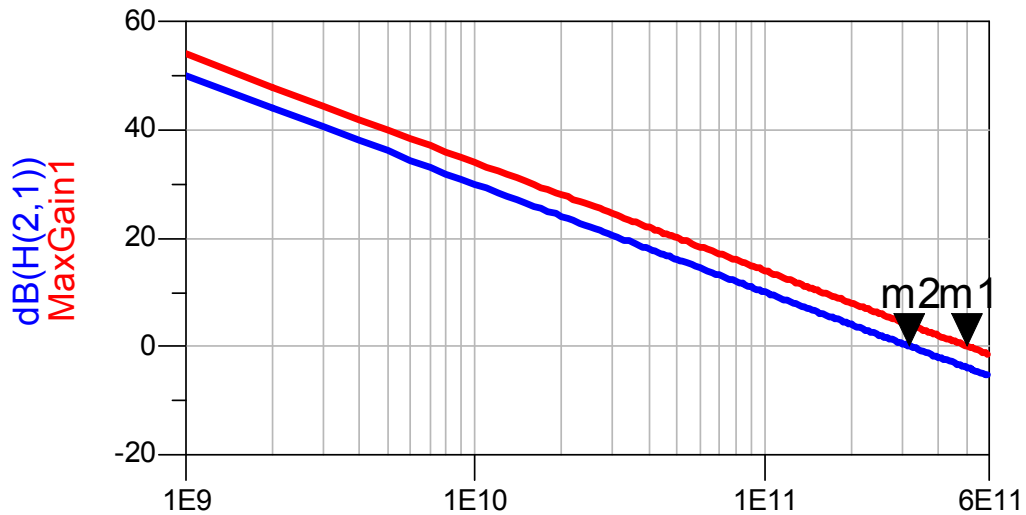

Eqn $H = \text{stoh}(S)$ freq, Hz

② For same unilateral device, set $W_g = 100 \mu\text{m}$.

Find Insertion Pwr gain, G_p , G_A , MAG .

$$g_m = 100 \text{ mS}$$

$$R_i = 10 \Omega$$

$$C_{gs} = 50 \text{ fF}$$

$$G_{DS} = 10 \text{ mS}, R_{DS} = 100 \Omega$$

Insertion gain = gain with 50Ω source & load impedance

$$\bullet G_i = \|S_{21}\|^2 \quad \bullet V_{out} = g_m V_{gs} (R_{DS} \| Z_0)$$

$$\bullet S_{21} = \frac{2 V_{out}}{V_{gen}} \quad \bullet V_{gs} = \frac{Y_{j\omega C_{gs}} \cdot V_{gen}}{R_i + Z_0 + Y_{j\omega C_{gs}}} = \frac{V_{gen}}{1 + j\omega C_{gs} (R_i + Z_0)}$$

$$\bullet V_{gen} = V_{gs} (1 + j\omega C_{gs} (R_i + Z_0))$$

$$S_{21} = \frac{2 g_m V_{gs} R_{DS} \| Z_0}{1 + j\omega C_{gs} (R_i + Z_0)} = \frac{2 (0.1) (33.3)}{1 + j 2\pi f (50 \times 10^{-15}) (60)} = \frac{6.666}{1 + j f (18.85 \text{ ps})}$$

$$S_{21} (100 \text{ GHz}) = 3.12$$

$$10 \log (3.12) = \boxed{9.88 \text{ dB} = G_i}$$

↳ because it's power gain

Operating Gain (G_p) = gain with input matched

As in ① $P_{in} = \omega^2 C_{gs}^2 V_{gs}^2 R_i$


$$P_{out} = I_{out}^2 R_L = \left(g_m V_{gs} \frac{R_{DS}}{R_{DS} + Z_0} \right)^2$$

$$G_p = \frac{P_{out}}{P_{in}} = \frac{g_m^2 V_{gs}^2 R_{DS}^2 Z_0}{(R_{DS} + Z_0)^2 \omega^2 C_{gs}^2 V_{gs}^2 R_i} \quad \text{Current divider} = \left(\frac{g_m R_{DS}}{(R_{DS} + Z_0) \omega C_{gs}} \right)^2 \times \frac{Z_0}{R_i}$$

$$= \left(\frac{.1 \times 100}{(150)(2\pi(100 \times 10^9)(50 \times 10^{-15}))} \right)^2 \frac{50}{10}$$

$$= 22.5$$

$$\boxed{G_p = 13.52 \text{ dB}}$$

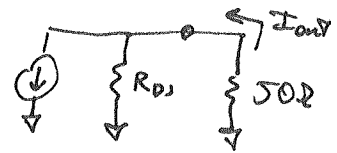

2) -cont.-

Available Pwr Gain $G_a = \text{Gain w/output matched} = \frac{P_{av,amp}}{P_{av,gen}}$

• $P_{out} = \frac{1}{4} g_m^2 V_{gs}^2 R_{DS}$ (same as MAG's P_{out})

• $V_{gs} = I_{in} / j\omega C$, • $I_{in} = \frac{V_{gen}}{Z_{in} + Z_0} = \frac{V_{gen}}{Z_0 + R_i + j\omega C}$

$V_{gs} = \frac{1}{j\omega C} \cdot \frac{V_{gen}}{Z_0 + R_i + j\omega C} = \frac{V_{gen}}{1 + j\omega C(R_i + Z_0)}$

So, $P_{out} = \frac{\frac{1}{4} g_m^2 V_{gen}^2 R_{DS}}{[1 + j\omega C(R_i + Z_0)]^2}$

$P_{in} = P_{av,gen} = \frac{1}{4} \frac{V_{gen}^2}{Z_0}$

$G_a = \frac{P_{out}}{P_{in}} = \frac{\frac{1}{4} g_m^2 V_{gen}^2 R_{DS} Z_0}{\frac{1}{4} V_{gen}^2 (1 + j\omega C(R_i + Z_0))^2} = \frac{g_m^2 Z_0 R_{DS}}{[1 + j\omega C(Z_0 + R_i)]^2}$

Evaluate @ 100 GHz, $|G_a| = 10.986$ $10 \cdot \log(10.986) = 10.4$

$G_a = 10.4 \text{ dB}$


MAG

$MAG = \frac{g_m^2 R_{DS}}{4\omega^2 C_{gs}^2 R_i} \Big|_{f=100\text{e}9} = \frac{(0.1)^2 100}{4(2\pi 100\text{e}9)^2 (50\text{e-}15)^2 10} = 25.3$

$MAG = 14 \text{ dB}$

Note: All of these gains can be found with S-parameters and Γ_1, Γ_2 in the general 2-port gain equations, depends only on your preference.

Problem #2

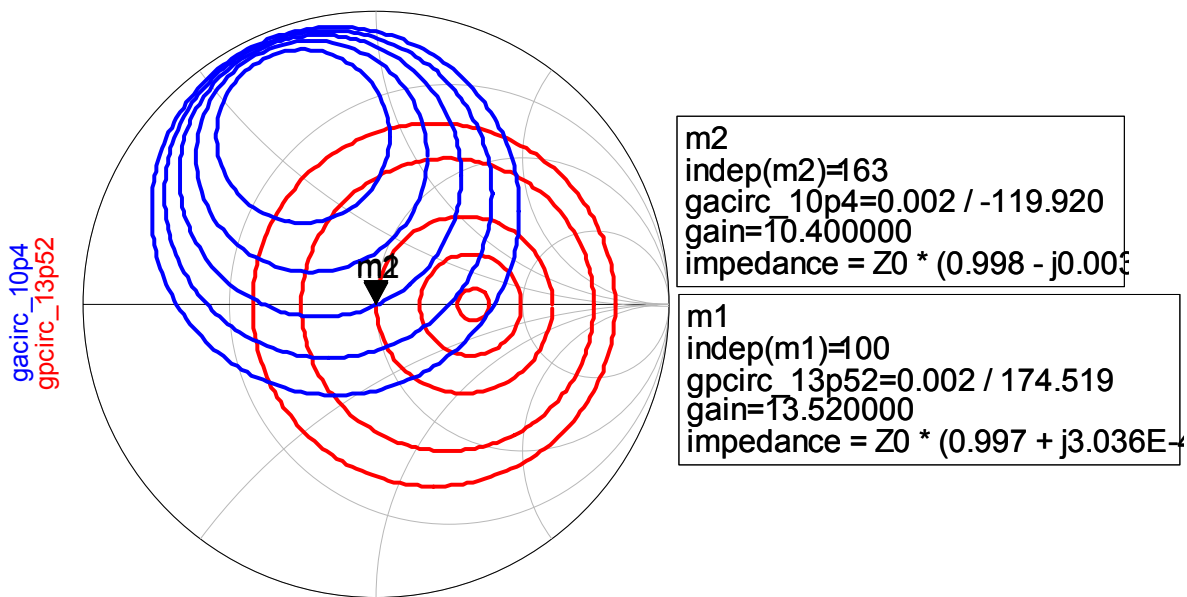

cir_pts (0.000 to 200.000)

Eqn gpcirc_13p52 = gp_circle(S,13.52 + {-2, -1, 0, 0.35, 0.5},200)
Eqn gacirc_10p4 = ga_circle(S,10.4 + {-2, -1, 0, 1, 2},200)


freq	db(S(2,1))	10*log(mag(S(2,1))^2)	MaxGain1
100.0 GHz	9.895	9.895	14.036

In the above displayed Ga and Gp circles, several gain values are plotted, above and below our calculated values for 50 ohm source and load impedance. We can see that the values of Ga and Gp determined in calculation occur for 50 ohm source and load impedance, respectively, because they pass through the center of the smith chart.


The insertion gain also matches well. This can be shown in two ways, as $10 \cdot \log(\text{mag}(S_{21})^2)$, using $10 \cdot \log$ because it is a power gain, or equivalently $\text{db}(S_{21})$, which is $20 \cdot \log(S_{21})$. These are mathematically identical. Max gain is also consistent with our calculation.

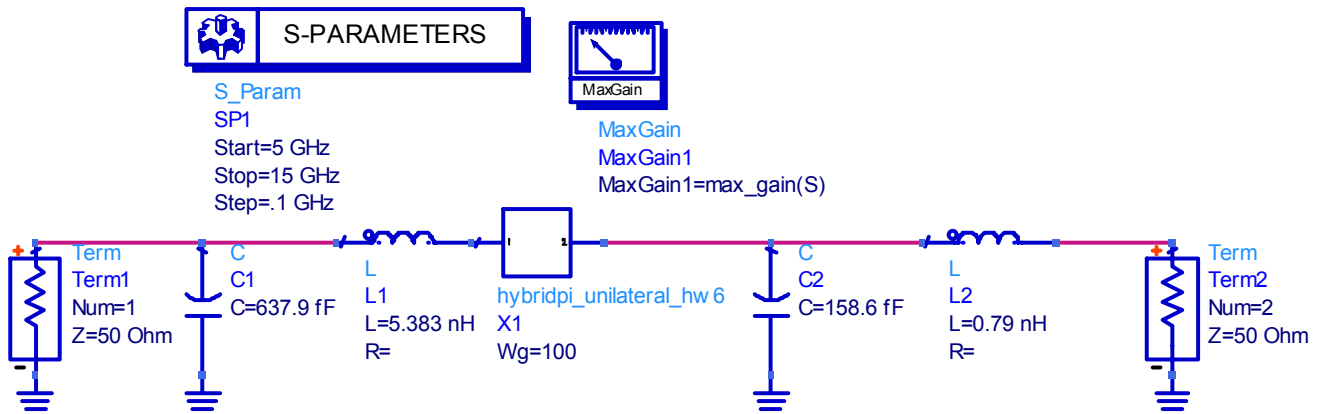Problem #3


Using ADS tuning, an LC matching network can be designed:



S11 and S22

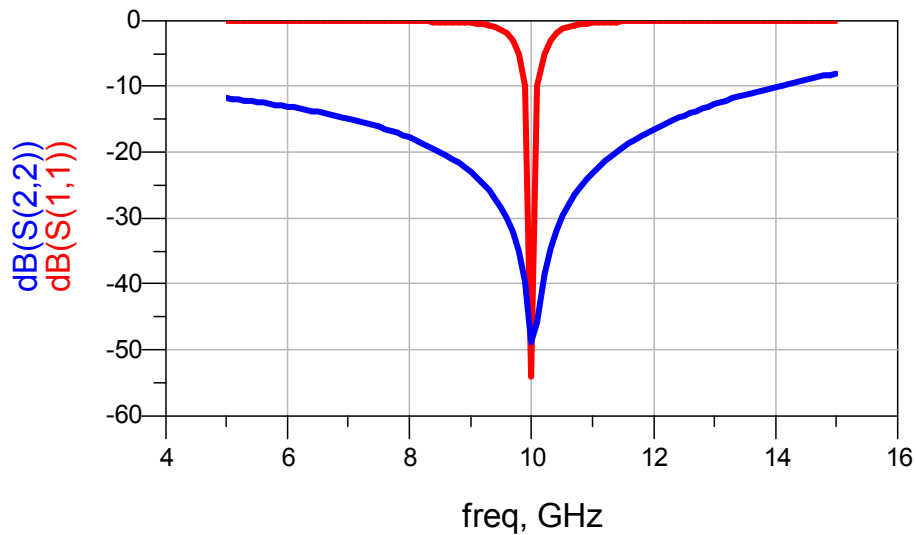


Gain:

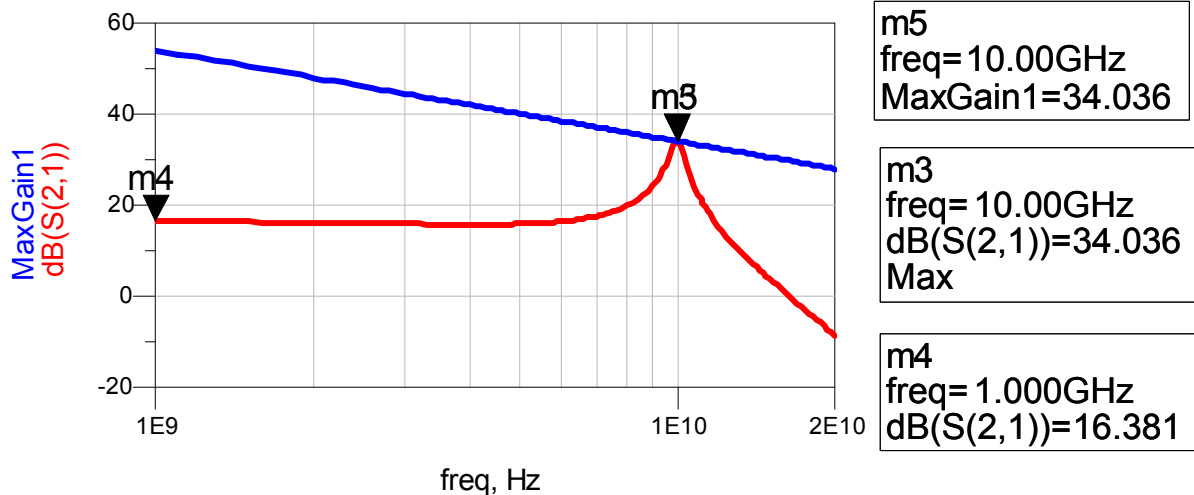

We can see that the gain when well-matched is equal to the maximum gain of the transistor, because the definition of maximum gain is when the input and output are both conjugate matched. The matching networks create an impedance equal to the conjugate of the input and output impedances.

4) Take bilateral device w/ $W_g = 100 \mu\text{m}$, find f_T , f_{max}
 $C_{gd} = 0.1 \frac{\text{fF}}{\mu\text{m}} \cdot W_g$ (other parameters same)

Start with finding H_{21} & f_T :

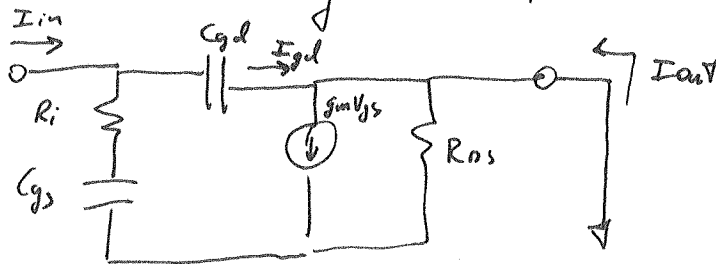

$$V_{gs} = I_{in} \left[(R_i + \frac{1}{j\omega C_{gs}}) \parallel \frac{1}{j\omega C_{gd}} \right] \cdot \frac{\frac{1}{j\omega C_{gs}}}{R_i + \frac{1}{j\omega C_{gs}}}$$

Voltage divider

$$= I_{in} \cdot \frac{(R_i + \frac{1}{s C_{gs}}) (\frac{1}{s C_{gd}})}{R_i + \frac{1}{s C_{gs}} + \frac{1}{s C_{gd}}} \cdot \frac{1}{1 + s C_{gs} R_i}$$

$$= I_{in} \cdot \frac{s C_{gs} (R_i + \frac{1}{s C_{gs}})}{s^2 R_i C_{gs} C_{gd} + s(C_{gs} + C_{gd})} \cdot \frac{1}{1 + s C_{gs} R_i}$$

$$V_{gs} = \frac{I_{in}}{s^2 R_i C_{gs} C_{gd} + s(C_{gs} + C_{gd})}$$

$$I_{out} = g_m V_{gs} - I_{gd}, \quad I_{gd} = I_{in} \cdot \left[(R_i + \frac{1}{j\omega C_{gs}}) \parallel \frac{1}{j\omega C_{gd}} \right] \cdot \frac{1}{\frac{1}{j\omega C_{gd}}}$$

Current Divider

$$= \frac{I_{in} (1 + s C_{gs}) s C_{gd}}{s^2 R_i C_{gs} C_{gd} + s(C_{gs} + C_{gd})}$$

$$I_{out} = \frac{g_m - (1 + s C_{gs}) s C_{gd}}{s^2 R_i C_{gs} C_{gd} + s(C_{gs} + C_{gd})} \cdot I_{in}$$

$$H_{21} = \frac{g_m - (1 + s C_{gs}) s C_{gd}}{s^2 R_i C_{gs} C_{gd} + s(C_{gs} + C_{gd})} \quad (\text{matches ADS})$$


$|H_{21}| = 1 @ f_T \rightarrow$ Challenging to solve by hand, solve with computer:

$$f_T = 318 \text{ GHz}$$

Note: same as unilateral case because R_i is not in series w/ both $C_{gs} + C_{gd}$

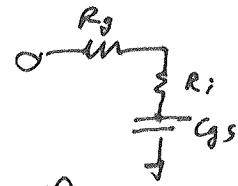4) -cont.-

Find f_{max} : Using eqn from Radwell's notes



$$f_{max} \approx \frac{f_r}{2\sqrt{(R_i + R_s + R_g) G_{DS} + 2\pi f_r R_g C_{gs}}}$$



once again, because $R_g = 0$
we get same as unilateral case

$$f_{max} = \frac{218 \text{ GHz}}{2\sqrt{10 \cdot \frac{1}{100}}}$$

$$f_{max} = 503 \text{ GHz}$$

(5)
(6)
(7) } see simulations & notes

Problem #4

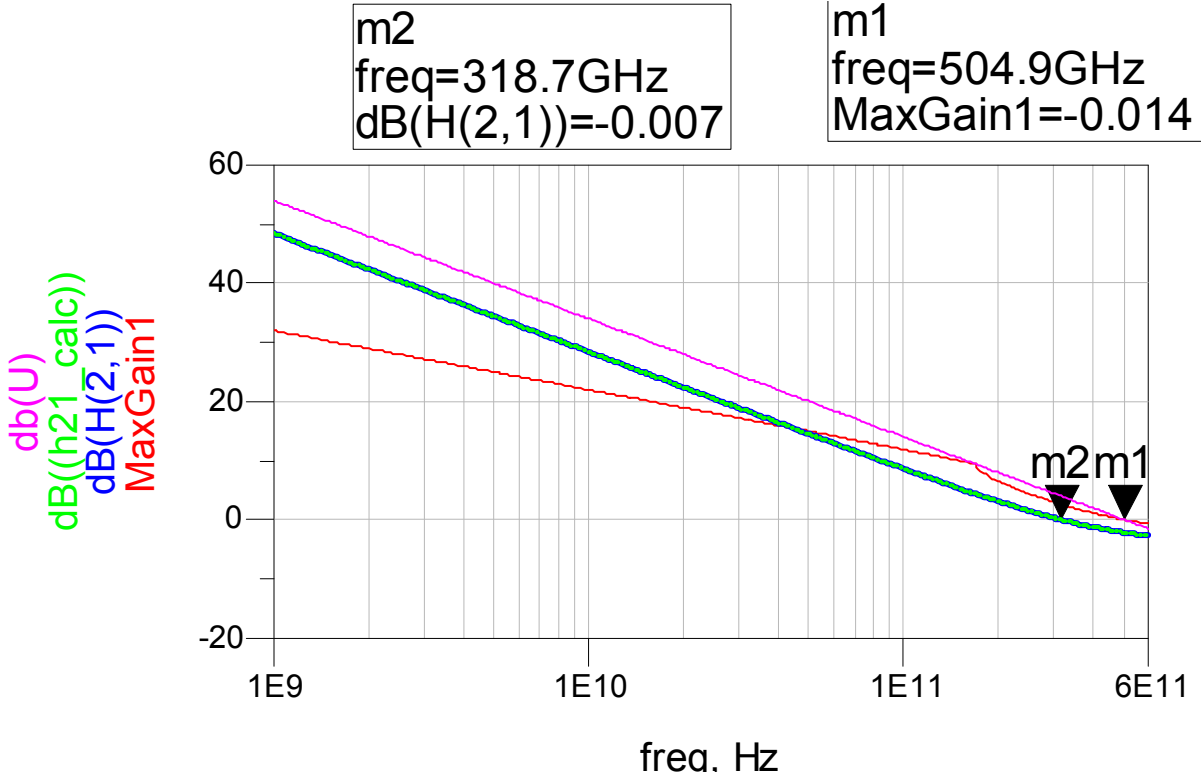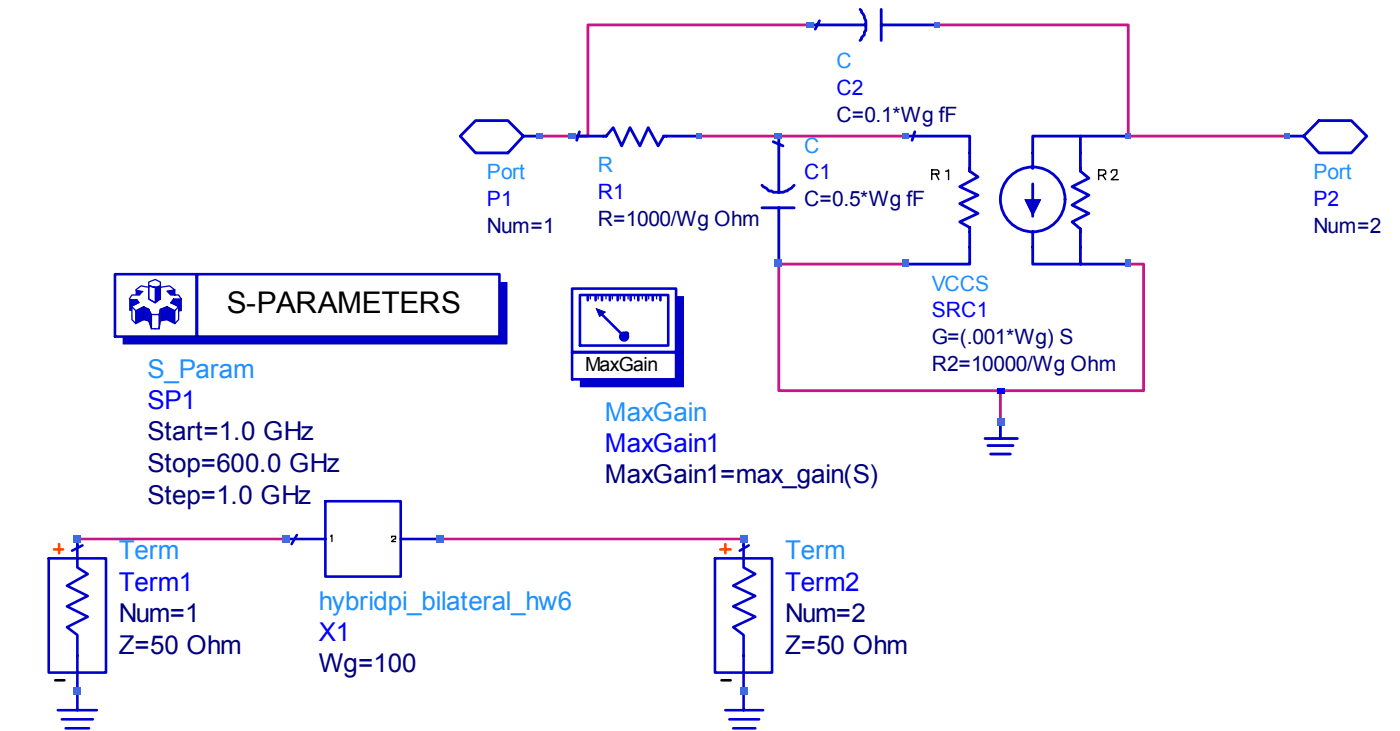

$$\text{Eqn } H = \text{stoh}(S)$$

$$\text{Eqn } \text{cgs} = .1\text{e-}15 * \text{wg}$$

$$\text{Eqn } \text{wg} = 100$$

$$\text{Eqn } \text{gm} = .001 * \text{wg}$$

$$\text{Eqn } \text{h21_calc} = (\text{gm} - (1 + \text{s} * \text{cgs} * \text{ri}) * \text{s} * \text{cgd}) / (\text{s} ** 2 * \text{ri} * \text{cgs} * \text{cgd} + \text{s} * (\text{cgs} + \text{cgd}))$$

$$\text{Eqn } \text{s} = \text{j} * 2 * \text{pi} * \text{freq}$$



$$\text{Eqn } \text{cgs} = .5\text{e-}15 * \text{wg}$$

$$\text{Eqn } \text{ri} = 1000 / \text{wg}$$

As we can see above, the calculated f_{max} and f_t match well with calculations. It is important to note that these values are the same as for the unilateral case, because in this case there is no R_g in series with both C_{GS} and C_{GD} .

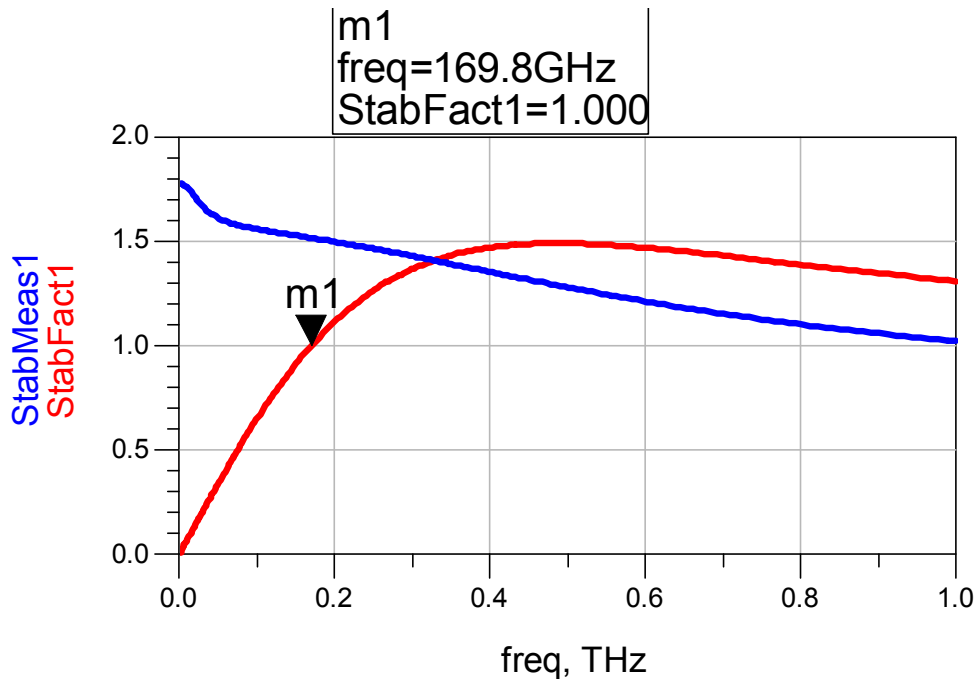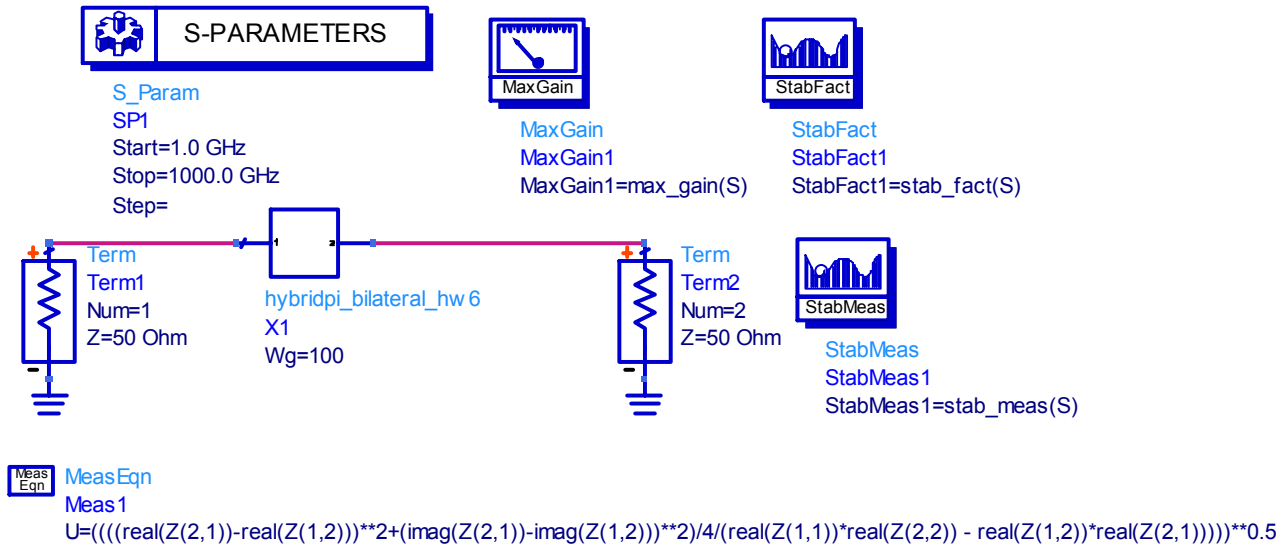
Problem #5

Plot stability factor K and B1 vs. frequency. It is necessary and sufficient for unconditional stability that $K > 1$ and $B1 > 0$. In ADS $k = stab_fact(S)$ and $B1 = stab_meas(S)$.



We can see that from DC-170GHz the transistor is potentially unstable, and it is unconditionally stable at all higher frequencies.

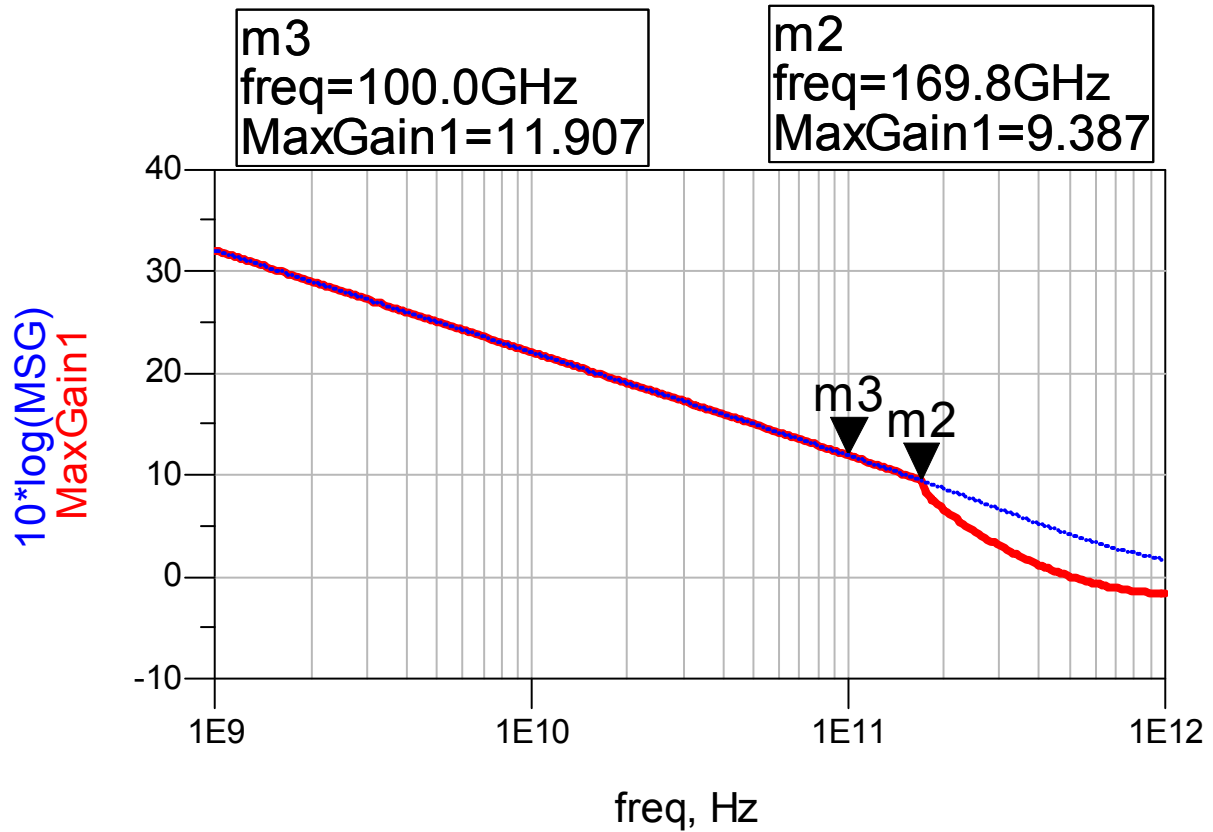
At a 100GHz we calculate the maximum stable gain, $\text{mag}(S_{21})/\text{mag}(S_{12})$ and plot it in ADS. We also plot the ADS `max_gain()` function, which will automatically switch from MAG to MSG when the transistor becomes unstable, and it matches with our calculation. The MSG at 100GHz is 11.9dB.



Eqn $\text{MSG} = \text{mag}(S(2,1))/\text{mag}(S(1,2))$

Problem #6

Stability circles at 100GHz:

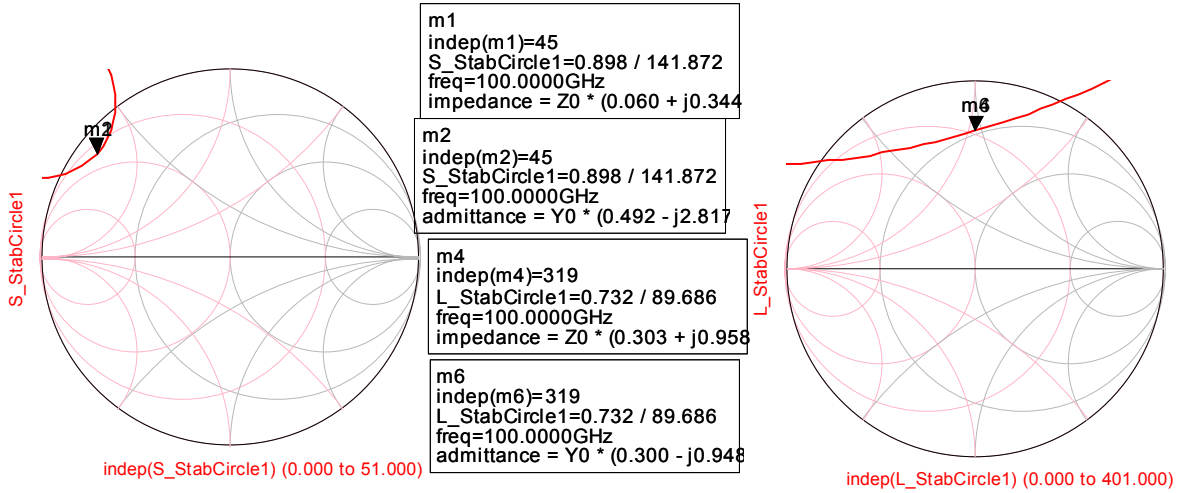


Input:

- Series R = $.06 * 50 = 3\Omega$
- Shunt R = $50 / .492 = 101.6\Omega$

Output:

- Series R = $.303 * 50 = 15.15\Omega$
- Shunt R = $50 / .3 = 166.67\Omega$

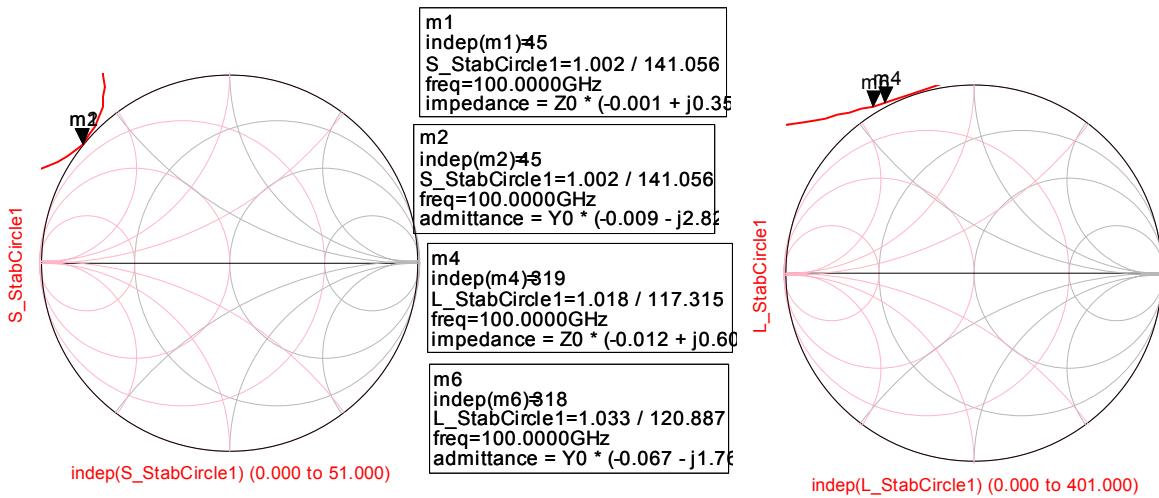
The first of these, series 3.1Ω on input, is shown. This value was used because 3Ω was very slightly not unconditionally stable, because the accuracy depends on how well we pick our point on the stability circle.



freq	StabFact1	StabMeas1
100.0 GHz	1.004	1.433

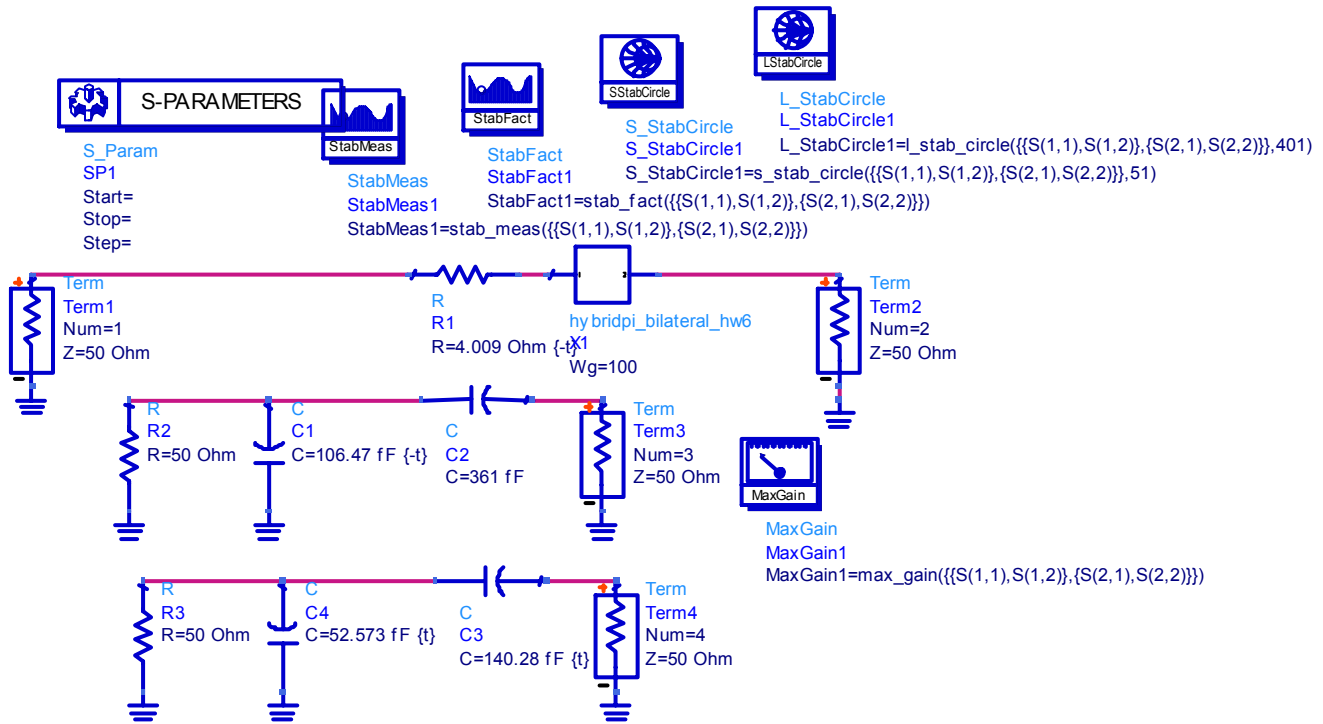Problem #7

As we found, MSG at 100GHz is 11.9dB. Use a series input resistor to stabilize with a value such that stabilized MAG = 9.9dB. This was found to be R=4Ω.



freq	MaxGain1	StabFact1	StabMeas1
100.0 GHz	9.907	1.108	1.402

Following are the gain circles used for calculating the matching network. The Ga circle specifies the allowable values of γ_s (reflection into transistor input from the matching network) for a given gain, and Gp circle does the same for γ_l . We select in this case γ_s as the MSG we designed for above, and with that we calculate $\gamma_{out} = S_{22} + S_{12} * S_{21} * \gamma_s / (1 - S_{11} * \gamma_s)$. Then to match we must choose γ_l as the complex conjugate of γ_{out} . This value of γ_l determines γ_{in} through a similar coupling equation, and because our transistor has been unconditionally stabilized, it is the conjugate of γ_s , so the input is also matched.

Therefore the gain is the MSG that we specified and the input and output reflections are very small, for our design frequency of 100GHz.


Eqn gacirc = ga_circle({S(1,1),S(1,2)},{S(2,1),S(2,2)}),MaxGain1 -{0,1,3,5},100)

Eqn gpcirc=gpc_circle({S(1,1),S(1,2)},{S(2,1),S(2,2)}),MaxGain1 -{0,1,3,5},100)


m2
 indep(m2)=100
 gacirc=0.862 / 139.779
 gain=9.907160
 impedance = Z0 * (0.084 + j0.364)

m4
 indep(m4)=0
 Gamma_S=0.862 / 139.779
 admittance = Y0 * (0.601 - j2.610)

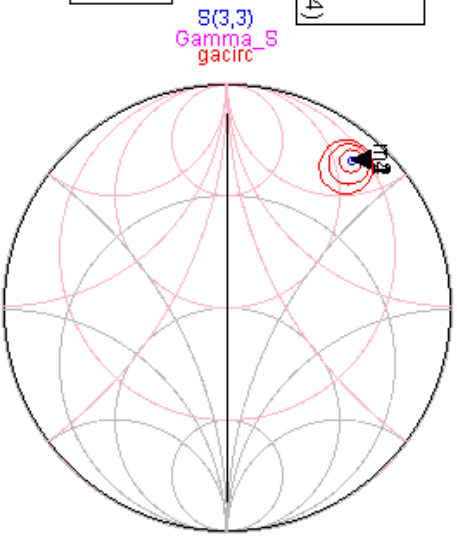m1
 freq=100.0GHz
 S(3,3)=0.862 / 139.788
 admittance = Y0 * (0.601 - j2.610)



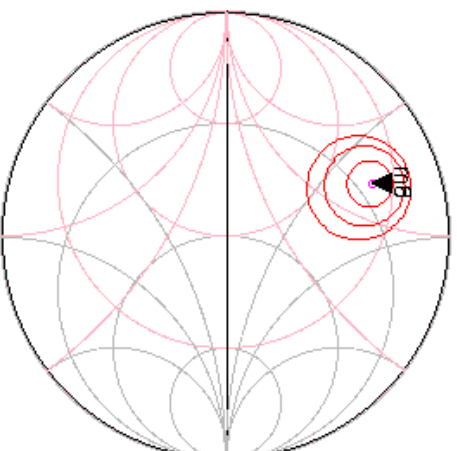ctr_pts (0.000 to 100.000)
 (0.000 to 0.000)
 freq (100.0GHz to 100.0GHz)



ctr_pts (0.000 to 100.000)
 freq (100.0GHz to 100.0GHz)

m3
 indep(m3)=100
 gpcirc=0.692 / 109.687
 gain=9.907160
 impedance = Z0 * (0.268 + j0.670)

m5
 freq=100.0GHz
 Gamma_L=0.692 / 109.687
 impedance = Z0 * (0.268 + j0.670)

m6
 freq=100.0GHz
 S(4,4)=0.692 / 109.640
 impedance = Z0 * (0.268 + j0.670)

Eqn Gamma_S=m2[0]

Eqn Gamma_in = conj(Gamma_S)

Eqn Gamma_L = conj(Gamma_out)

Eqn Gamma_out = S22+S12*S21*Gamma_S/(1-S11*Gamma_S)

Eqn Gamma_in2 = S11+S12*S21*Gamma_L/(1-S22*Gamma_L)

freq	Gamma_L	Gamma_out	Gamma_S	Gamma_in
100.0 GHz	0.692/-109.687	0.692/-109.687	0.862/139.779	0.862/-139.779

